

1.

Code:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity cnt is
6  port(
7      clk, res: in std_logic;
8      Q: out std_logic_vector(3 downto 0)
9  );
10 end cnt;
11
12 architecture cnt of cnt is
13     signal nowt: std_logic_vector(3 downto 0);
14     signal m: std_logic;
15 begin
16     process(clk, res)
17     begin
18         if res = '1' then
19             m <= '1'; nowt <= "0000";
20         elsif clk'event and clk = '1' then
21             if nowt = "1111" and m = '1' then
22                 nowt <= nowt - 1;
23                 m <= '0';
24             elsif nowt = "0000" and m = '0' then
25                 nowt <= nowt + 1;
26                 m <= '1';
27             elsif m = '1' then nowt <= nowt + 1;
28             elsif m = '0' then nowt <= nowt - 1;
29             end if;
30         end if;
31     end process;
32     Q <= nowt;
33 end cnt;
34
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  Ⓜentity decoder is
6  Ⓜ    port(
7      |      input: in std_logic_vector(3 downto
8      |      F: out std_logic_vector(15 downto 0)
9      |    );
10 |  end decoder;
11 |
12 Ⓜarchitecture decoder of decoder is
13 Ⓜbegin
14 |
15 |      F <= x"0001" when input = x"0" else
16 |          x"0002" when input = x"1" else
17 |          x"0004" when input = x"2" else
18 |          x"0008" when input = x"3" else
19 |          x"0010" when input = x"4" else
20 |          x"0020" when input = x"5" else
21 |          x"0040" when input = x"6" else
22 |          x"0080" when input = x"7" else
23 |          x"0100" when input = x"8" else
24 |          x"0200" when input = x"9" else
25 |          x"0400" when input = "1010" else
26 |          x"0800" when input = "1011" else
27 |          x"1000" when input = "1100" else
28 |          x"2000" when input = "1101" else
29 |          x"4000" when input = "1110" else
30 |          x"8000" when input = "1111" else
31 |          x"0000";
32 |
33 end decoder;


```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity cnt_decoder is
6  port(
7      clk, res: in std_logic;
8      F: out std_logic_vector(15 downto 0)
9  );
10 end cnt_decoder;
11
12 architecture cnt_decoder of cnt_decoder is
13     signal cntout: std_logic_vector(3 downto 0);
14     component cnt is
15     port(
16         clk, res: in std_logic;
17         Q: out std_logic_vector(3 downto 0)
18     );
19     end component;
20
21     component decoder is
22     port(
23         input: in std_logic_vector(3 downto 0);
24         F: out std_logic_vector(15 downto 0)
25     );
26     end component;
27
28 begin
29     U1: cnt port map(clk, res, cntout);
30     U2: decoder port map(cntout, F(15 downto 0));
31 end cnt_decoder;

```

模擬:

 

2.

Code:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity BCD is
6  port(
7      clk, res, Cin: in std_logic;
8      Q: out std_logic_vector(3 downto 0);
9      Cout: out std_logic
10 );
11 end BCD;
12
13 architecture BCD of BCD is
14     signal nowt: std_logic_vector(3 downto 0);
15 begin
16     process(clk, res, Cin)
17     begin
18         if res = '1' then nowt <= "0000";
19         elsif clk'event and clk = '1' and Cin = '1' then
20             if nowt = "1001" then
21                 nowt <= "0000";
22             else nowt <= nowt + 1;
23             end if;
24         end if;
25     end process;
26     Q <= nowt;
27     Cout <= '1' when nowt = "1001" and Cin = '1' else '0';
28 end BCD;
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity BCD_counter is
6  port(
7      clk, res: in std_logic;
8      result1, result2, result3: out std_logic_vector(3 downto 0);
9      result: out std_logic_vector(11 downto 0)
10 );
11 end BCD_counter;
12
13 architecture BCD_counter of BCD_counter is
14     component BCD is
15     port(
16         clk, res, Cin: in std_logic;
17         Q: out std_logic_vector(3 downto 0);
18         Cout: out std_logic
19     );
20     end component;
21     signal sum1, sum2, sum3: std_logic_vector(3 downto 0);
22     signal Ci, Co: std_logic_vector(2 downto 0);
23 begin
24     Ci(0) <= '1';
25     Ci(1) <= Co(0);
26     Ci(2) <= Co(1);
27
28     U1: BCD port map(clk, res, Ci(0), sum1, Co(0));
29     U2: BCD port map(clk, res, Ci(1), sum2, Co(1));
30     U3: BCD port map(clk, res, Ci(2), sum3, Co(2));
31
32     result1 <= sum1;
33     result2 <= sum2;
34     result3 <= sum3;
35     result <= sum3 & sum2 & sum1;
36
37 end BCD_counter;

```

模擬:

